

AN-1651 Keeping Up with the Expanding Demands of High-Performance Audio

ABSTRACT

This application report provides several design examples of high-performance applications using the LME49710/LM4562 that demonstrate their capability in meeting the demands of the highest audible performance.

Contents

1	Introduction	2
2	RIAA Phono Pre-Amplifier	2
3	RIAA Equalization	3
3.1	RIAA Phono Pre-Amplifier: Topology 1 – Passive EQ	4
3.2	Gain Distribution	4
3.3	Cartridge Loading	5
3.4	RIAA Equalization Network	5
4	RIAA Phono Pre-Amplifier: Topology 2 – Active / Passive EQ	5
5	Electrostatic Headphone Amplifier	6
6	Bibliography	9

List of Figures

1	RIAA Equalization Response.....	3
2	Passive EQ RIAA Phono Pre-Amplifier Topology	4
3	Active/Positive Phono Pre-Amplifier Topology	5
4	Typical ESL Construction	7
5	ESL Operating Principle.....	7
6	ESL Amplifier Schematic.....	9

List of Tables

1	RIAA Equalization Response.....	3
---	---------------------------------	---

1 Introduction

Engineers designing audio equipment for the high-end audiophile or professional recording markets have a limited selection of high-resolution signal amplifiers that will meet end-user demands for both outstanding objective and critical subjective performance. Suitable devices must provide a combination of state-of-the-art specifications for low noise and ultra-low distortion along with high GBP and preferably unity gain stability. While nearly all suppliers develop and provide devices optimized for video, instrumentation, or low power, these applications demand a specification mix that does not necessarily align with the needs of the high-performance audio engineer. Accordingly, Texas Instruments has developed a series of high-performance, high-fidelity audio amplifiers specifically optimized for these applications.

The LME49710 / LM4562 are representative of this line of devices and have been optimized for the high performance and professional community. They provide the designer with unprecedented levels of THD (0.00003%) and IM (0.00005%) plus very low noise (2.7 nV / $\sqrt{\text{Hz}}$) and GBWP of 55 MHz with output current of ± 26 mA into a 600 Ω load. Supply current is extremely low, serving the needs of both portable products as well as multimedia components utilizing multiple amplifiers.

Note that the design philosophy and choices discussed herein will frequently refer to the practices embraced by the professional and high-performance community as having both objective (measurable) as well as subjective (audible) merit. The quantification of the contribution of these techniques has been published in many other documents and will not be included in this document. Included in this approach are capacitor dielectric choices, power supply impedance considerations, and circuit topology.

Objectively, it is understood that best practices are required with device parameter consideration relative to circuit topology as well as grounding/shielding practices, power supply purity, and other well documented practices generally applied to sensor conditioning and instrumentation applications.

2 RIAA Phono Pre-Amplifier

Phono amplifiers are utilized to amplify and equalize to the RIAA standard signal from magnetic phono cartridges. Although phono cartridge technology can be based on several forms of electrical generation, but in rare cases the highest quality are electro-magnetic using either a fixed coil (moving magnet) or fixed magnet (moving coil) designs. The moving magnet designs provide higher output voltages generally in the region of 1.0 mV for each cm/s tip of recorded velocity while moving coils deliver 0.1 mV under the same circumstances. Although this would seem to indicate that moving magnet is preferred (at least from the standpoint of the pre-amp designer), it is commonly accepted that the moving coil configuration provides superior audible performance most likely due to the lower mass of the cantilever assembly.

The key parameters of concern with RIAA equalized phono pre-amplifiers are low noise, low total harmonic distortion, low intermodulation distortion, and bandwidth. When interfacing with low output moving coil cartridges with source impedances of less than 100 Ω , the first amplifier should target an input noise voltage density of < 5 nV / $\sqrt{\text{Hz}}$. Of course, THD and IMD should be as low as possible.

Although not commonly emphasized, a high PSRR across the full signal bandwidth is critical to the audible performance of the circuit. While the more commonly discussed specifications of distortion, noise, bandwidth and slew rate are important to characterize the performance of the amplifier, if one envisions an audio amplifier as a device that modulates the power supply current into the load in direct response to the input signal, it is clear that the power supply rails must present a low and more importantly flat impedance across the audio bandwidth to preserve the audible spectral balance and overall integrity of the input signal. The PSRR of the LME49710/ LM4562 is outstanding across the full audio bandwidth and therefore is highly immune to power supply impedance discontinuities. However, given the low level signals provided from moving coil phono cartridges, the effect is more pronounced and therefore the impedance of the supply rails is addressed in this application.

In order to avoid the distortion contribution of coupling capacitors, the two circuit topologies presented will use direct coupling from input to output. Overall DC gain will be 74 dB (44 + 30) for the fully passive EQ design and 70 dB (44 + 26) for the active-passive EQ design. Typical V_{OS} of the LME49710 is 0.05 mV while I_{bias} is 7 nA. With the aforementioned DC gain, voltage offset at the output will typically be less than 1 volt. To compensate and provide for full DC coupling, servo offset amplifier U3 has been included.

Although we will not be discussing a fully active RIAA design, when this topology is used, the demands on slew rate and unity gain stability will intensify.

3 RIAA Equalization

Table 1 shows the RIAA equalization response while Figure 1 displays the same graphically. The response is normally defined relative to 1 kHz with approximately 20 dB rise and attenuation relative to this frequency. The total dynamic range is actually greater than 40 dB as the high frequency rolloff continues beyond the second high-frequency inflection point (2.122 kHz) beyond audibility.

Table 1. RIAA Equalization Response

Frequency	Amplitude	Frequency	Amplitude
20	19.3	800	0.7
30	18.6	1000	0
40	17.8	1500	-1.4
50	17	2000	-2.6
60	16.1	3000	-4.8
80	14.5	4000	-6.6
100	13.1	5000	-9.6
150	10.3	6000	-8.2
200	8.2	8000	-11.9
300	5.5	10000	-13.7
400	3.8	15000	-17.2
500	2.6	20000	-19.6

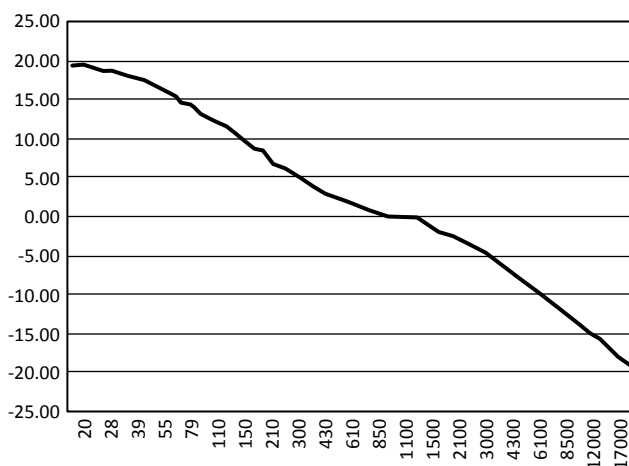


Figure 1. RIAA Equalization Response

Much has been written about the audibility of even minor departures from the ideal RIAA equalization and consequently high performance consumer and professional markets demand a high degree of accuracy. These pursuits have led to a preponderance of topologies in both the active equalization and passive equalization schemes as well as active/passive approaches. Recent papers have pursued the math and have provided design guides to determine the precise values for these topologies and therefore we will not repeat that work in this application report.

Although there are several common circuit topologies for realizing a RIAA phono pre-amplifier, we will be confining our discussion to two topologies popular with the high performance community. These are the fully passive topology as shown in Figure 2 and the hybrid passive/active topology as shown in Figure 3.

Note that it is possible to include a very low frequency rolloff to filter out room induced and turntable mechanical contributions however given that this represents a departure from the ideal, we will not include a discussion in this paper. The reader however may incorporate this filter with the inclusion of a capacitor in the feedback leg to ground of R7.

3.1 RIAA Phono Pre-Amplifier: Topology 1 – Passive EQ

Figure 2 shows the circuit topology for a RIAA phono preamplifier with passive equalization capable of interfacing with a low output moving coil cartridge.

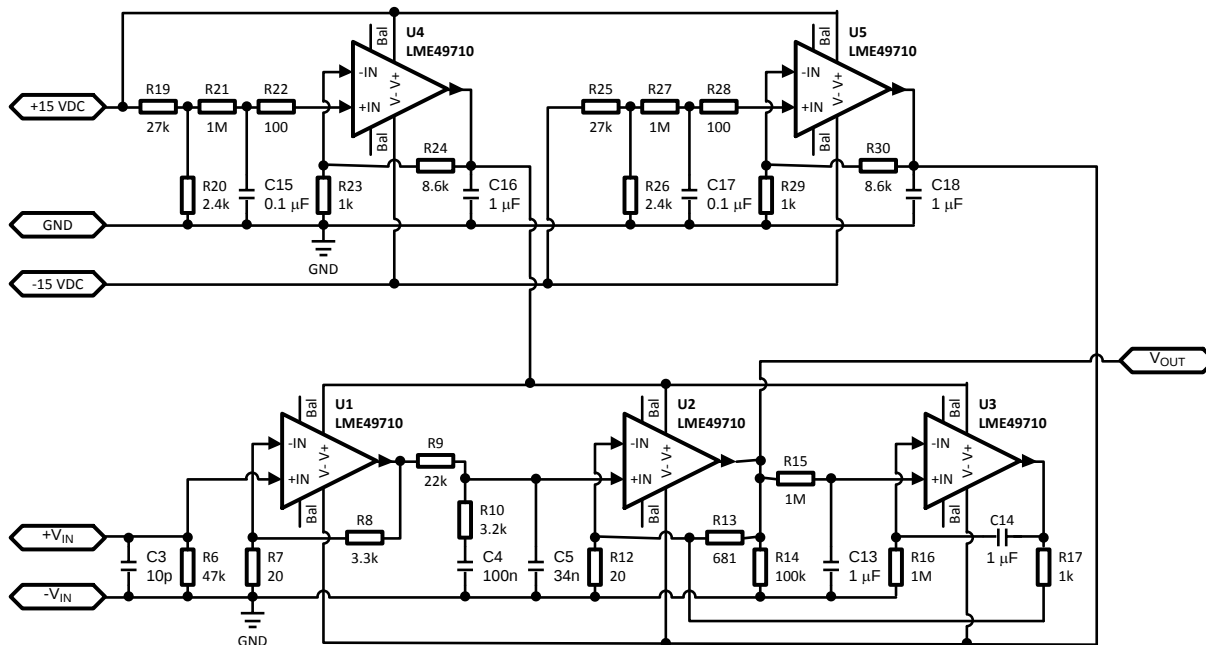


Figure 2. Passive EQ RIAA Phono Pre-Amplifier Topology

3.2 Gain Distribution

The gain distribution of the design is defined by two issues – noise and input overload margin. To achieve the best noise performance, it is preferable to have high gain in stage U1 with the balance in stage U2. Alternatively from an overload perspective, the opposite distribution is preferred. By using high supply voltages it is possible to extend the gain of the first stage to 44 dB and minimize overload concerns especially with lower output moving coil cartridges. (If moving magnet cartridges are being used, it may be beneficial lower the gain of the first stage by 10 to 15 dB.) In order to meet a target mid band (1 kHz) gain of approximately 55 dB, the gain of the second stage has been configured to be approximately 30 dB (44 dB + 30 dB -20 dB at midband). To completely eliminate coupling capacitors in the signal path the design is fully direct coupled. Servo amplifier U3 has been included to compensate for voltage offset errors and assure near zero voltage at the output.

3.3 Cartridge Loading

All cartridge suppliers provide specific resistive and capacitive loading recommendations and these should be included in the design for the specific cartridge chosen. Moving coil cartridge loading is generally in the region of 100Ω paralleled by a 100 pF capacitor, while moving magnet cartridges typically require 47Ω combined with a 300 pF capacitor. The schematic shown defines a 47Ω resistor in parallel with a 100 pF capacitor on board and therefore the builder may trim the load as specified (both resistive and capacitive) as specified by the cartridge manufacturer by soldering the needed resistor and capacitor at the input connector terminals. Generally, with moving coil cartridges, a good starting point would be 100Ω (combined with the 100 pF already on board).

3.4 RIAA Equalization Network

The network chosen to provide the RIAA equalization, shown graphically in Figure 1 consist of components R9, R10, C4, and C5. The values shown are based upon the work of Lipshitz¹ and represent the nearest EIA standard values. Low DA and DF capacitors such as Polystyrene or polypropylene are strongly recommended. To quantify the departure from ideal, the design was both simulated with PSpice and subsequently built then measured using an inverse RIAA filter² at the input. The inverse RIAA design is described in Reference 2. We encourage the designer to fabricate this inverse network not only to verify simulations but also as a very convenient device to perform both objective and subjective evaluations on both this design and others as well. In this manner, signal sources other than pure phono cartridges can be used as source material.

4 RIAA Phono Pre-Amplifier: Topology 2 – Active / Passive EQ

Figure 3 shows the circuit topology for a RIAA phono pre-amplifier using a combination of both active and passive equalization capable of interfacing with a low output moving coil cartridge.

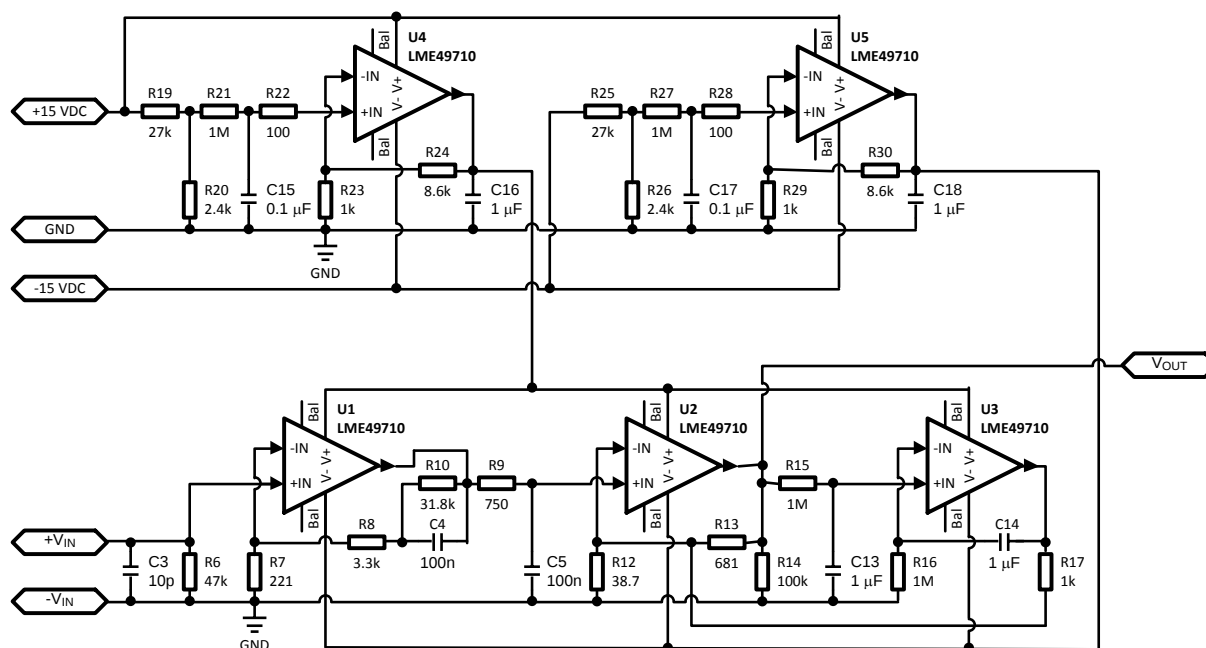


Figure 3. Active/Positive Phono Pre-Amplifier Topology

The first stage (U1) in combination with feedback components R8, R9, and C4 establishes the first two RIAA EQ time constants (3180 μ S and 318 μ S). This stage also provides a midband (1 kHz) gain of approximately 27 dB. Note that the DC gain of this stage is 44 dB as in the case of the fully passive topology design first stage.

The final RIAA EQ time constant (75 μ S) is obtained passively between stage 1 and stage 2 from components R9 and C5. Stage 2 (U2) provides a gain of approximately 25 dB. The result is a midband gain of approximately 52 dB and a DC gain of approximately 70 dB. As with the fully passive design, U3 is included as a DC servo amplifier to ensure near 0 V_{DC} at the output.

5 Electrostatic Headphone Amplifier

By a significant margin, the most common loudspeaker transducer used today is based upon electromagnetic principles. These “speaker drivers” typically take the form of a round rigid “cone” loosely suspended at its perimeter driven by a “voice coil” which surrounds a fixed magnet. The cone is driven into motion from current delivered to the voice coil. Two contradicting requirements – high cone stiffness and low assembly mass limit the performance of these designs (although planar and ribbon designs have reduced these issues in exchange for increasing costs).

By contrast, electrostatic loudspeaker transducers (see [Figure 4](#)) provide a deflection force to a 3 to 5 mil suspended diaphragm (usually mylar) using electrostatic forces. The (slightly) conductive diaphragm (approximately 10 Ω /sq) is suspended between two acoustically transparent “stators” which themselves are driven by a high voltage out of phase audio signal (see [Figure 5](#)). The diaphragm is biased with a high voltage (level dependent upon relative physical distances) relative to the stators. The result is a push-pull force exerted on the diaphragm across the entire surface displaces the surrounding air. The stators are usually insulated to prevent arching if and when the diaphragm approaches the stators. In theory, the superiority of the electrostatic transducer is due to the low mass of the diaphragm (approaching the mass of air), the application of the force across the entire surface, and the push-pull force that reduces even harmonic distortion. As a result, properly designed electrostatic transducers will provide low distortion, outstanding transient response, and wide bandwidth compared to even planar magnetic designs. This superior audible performance is not without both electrical and acoustical challenges including limited dynamic range (limited by the full excursion of the diaphragm), low frequency rolloff (due to their bi-polar room coupling), high-frequency beaming (inversely proportional to the width of the diaphragm), and the need to provide low distortion, large voltage excursions. Headphones minimize these challenges due to their controlled acoustical environment, small size, and low output requirements. Consequently, properly designed ESL headphones (along with careful attention to the driving means) are capable of the most audibly transparent audio reproduction (neglecting the loss of room special cues) available.

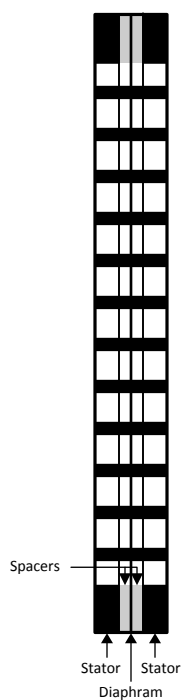


Figure 4. Typical ESL Construction

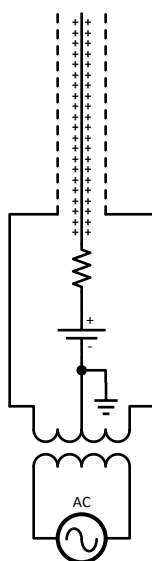


Figure 5. ESL Operating Principle

The electrostatic transducer used in nearly all commercial designs is a push-pull constant charge design where a diaphragm is placed within a uniform electric field. A high resistivity coating is applied to the diaphragm to provide for a constant charge across its surface. The superior linearity of this design has been described in detail previously 3,4,5 where it has been shown that an ESL can be theoretically free of distortion when the charge on the diaphragm remains constant as it moves between the stators. Under these circumstances, the force on the diaphragm will be defined by:

- $F = Q \times E(t)$ (newtons)
where $Q = 2eAV / d$ (coulombs)
- $E(t) = v(t) / 2d$ (volts / meter)
- $C = eA / d$ (farads)
therefore, $F = CVv(t) / d$ (newtons)
where C = capacitance of the transducer (diaphragm to stator)
- V = Bias Voltage (volts)
- $v(t)$ = time varying signal
- d = diaphragm to stator spacing (meters)
- A = Diaphragm Area (sq-meters)
- $e = 8.85 \times 10^{-12}$ (farads / meter)

The electrostatic transducer is primarily capacitive in nature (in contrast to the low impedance, mostly resistive- inductive, load of the electromagnetic transducer) and therefore demands a source capable of delivering suitable charging currents. Because the predominance of commercial loudspeakers are electromagnetic based, all commercial amplifiers are designed to interface with these low-impedance loads. Accordingly, all electrostatic loudspeaker manufacturers provide the needed bias voltage and voltage amplification in the form of an add-on "interface unit" typically consisting of a bias supply and step up transformer with a suitably high step up ratio (Figure 5). Unfortunately, it is difficult to design a wide band transformer with superior performance when high step-up ratios are required. A superior solution is to drive the stators directly with a large voltage swing, wide bandwidth amplifier capable of delivering the current necessary to support the capacitive load imposed by the transducer.

The design presented in Figure 6 will deliver nearly 200 Vp-p across the full audio bandwidth when interfaced to the popular Stax type 1 electrostatic headphones. A bias of 200 V_{DC} is shown although the resistive divider can be altered to provide a bias voltage up to 400 V_{DC}. Note that many of the Stax type 1 headphones have similar drive and bias requirements making this design suitable for these models as well.

From Figure 5 it is clear that a balanced high-voltage drive is needed. In this design, one half of the LM4562 is used to drive to a discrete differential amplifier using a pair of high voltage N-Channel MOSFETs. An LM317 is used in a current source mode to insure that the CMRR remains above 60 dB. The second half of the LM4562 is used as a servo amplifier. This servo actively compensates for the fully DC feedback via R7 to insure that the output of U1A will remain at 0 V_{DC} needed to keep the differential amplifier Q1 and Q2 properly biased for maximum V_{out}. Potentiometer R11 allows for variation in MOSFETs and must be adjusted to have 0 V_{DC} difference across Q1 and Q2 drain terminals. For best performance regulated sources should be used for the 400 V_{DC} and dual 15 V_{DC} supplies.

The design is fully DC-coupled from input to the output but for the output coupling capacitors. Using the highest quality capacitors (polypropylene, polystyrene or Teflon) will result in the highest audible performance.

It should be noted that several alternate designs were built and auditioned including fully differential topologies however the most musical audible performance was achieved using the topology shown.

Note that it is possible to directly substitute a 6FQ7/6CG7 miniature triode or 6SN7 octal triode in place of the MOSFETs if a tube output stage is desired. In this case, a suitable filament supply will be required.

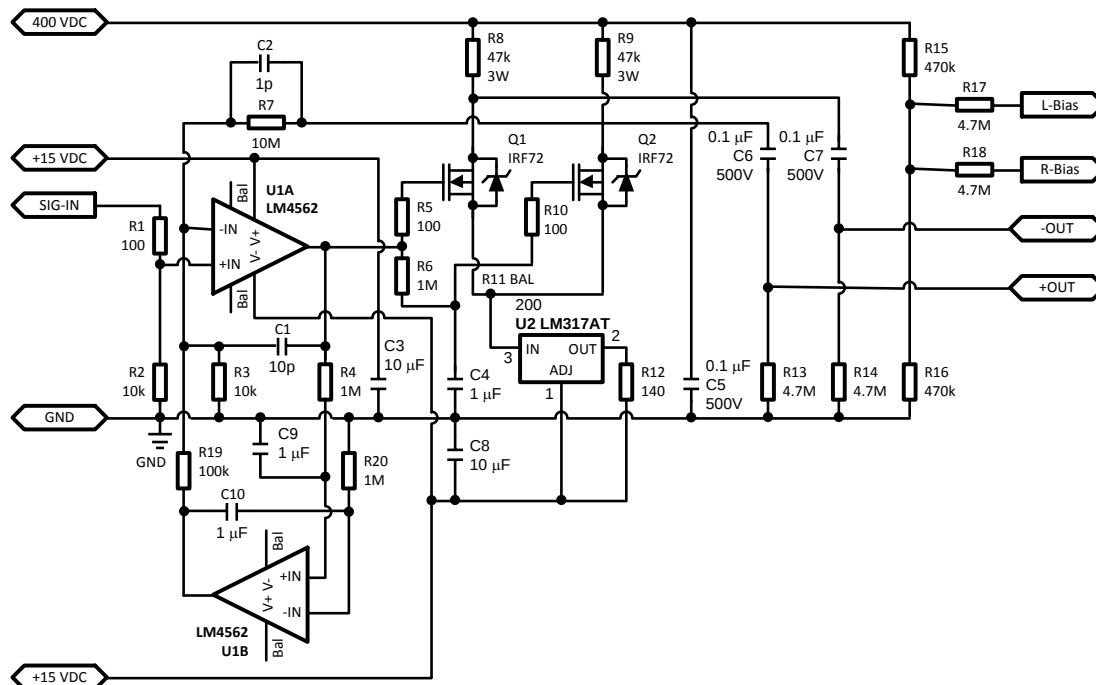


Figure 6. ESL Amplifier Schematic

6 Bibliography

1. Lipshitz, S.J., "On RIAA Equalization Networks," JAES Vol 27, No 6, June 1979, pp 458 – 481
2. Lipshitz, Stanley and Jung, Walt, "A High Accuracy Inverse RIAA Network," The Audio Amateur, 1/ 1980
3. Vogt, Hans, "Recent Developments in the Design of Electrostatic Loudspeakers," Radio News, 13, 656 (1932)
4. Walker, P.J., "Wide range Electrostatic Loudspeakers," Wireless World, 41, 20S (1955)
5. Janzen, A.A., Pritchard, R.L., and Hunt, F.V., Electrostatic Loudspeakers, (Office Naval Research NR-014-903, T.M. 17), Cambridge: Harvard University (Acoustics research Laboratory), 1950

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Applications Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Automotive and Transportation	www.ti.com/automotive
Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Video and Imaging	www.ti.com/video

TI E2E Community

e2e.ti.com